

2. الجهد الكهربائي $V(H)$

$$\begin{aligned} V(H) &= V_A + V_B + V_C + V_D \\ &= \frac{kq_A}{a} + \frac{kq_B}{r} + \frac{kq_C}{r} + \frac{kq_D}{a} \\ &= \frac{kq}{a} + \frac{k(-5q)}{\sqrt{5}a} + \frac{k(-5q)}{\sqrt{5}a} + \frac{kq}{a} \\ &= \frac{2kq}{a} - \frac{10kq}{\sqrt{5}a} = \frac{kq}{a} \left(2 - \frac{10}{\sqrt{5}} \right) \end{aligned}$$

$$\boxed{V(H) = \frac{2kq}{a} \left(1 - \frac{5}{\sqrt{5}} \right)}$$

3. شدة القوة الكهربائية $\vec{F}(H)$

$$\vec{F}_H = q_H \cdot \vec{E}_H = -5q \cdot \frac{4}{\sqrt{5}} \frac{kq}{a^2} \vec{\lambda}$$


$$= -\frac{5 \cdot 4}{\sqrt{5}} \cdot \frac{kq^2}{a^2} \vec{\lambda} \Rightarrow \boxed{\vec{F}_H = -4\sqrt{5} \frac{kq^2}{a^2} \vec{\lambda}}$$

4. الطاقة الكامنة للشحنة q_H

$$E_{p_{q_H}} = q_H \cdot V_H = -5q \cdot \frac{2kq}{a} \left(1 - \frac{5}{\sqrt{5}} \right)$$

$$\boxed{E_{p_{q_H}} = \frac{10kq^2}{a} \left(\frac{5}{\sqrt{5}} - 1 \right)}$$

حل التمرين (02):

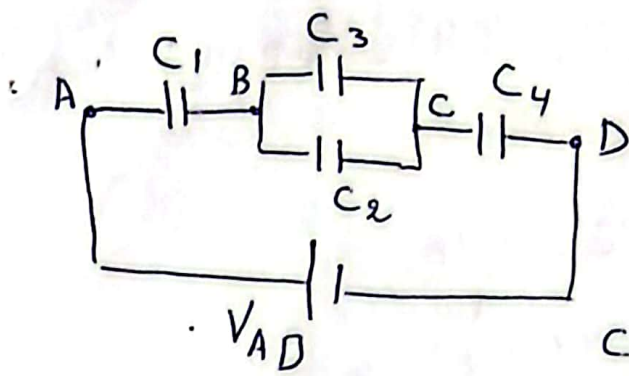

1- السعة المكافئة: C_{eq}

- C_2 و C_3 على التفرع

$$= 5 + 15 = 20 \mu F$$

$$C_{eq1} =$$

$$C_{eq1} = 20 \mu F$$

C_1 و C_{eq1} على التسلسل:

$$C_{eq2} = \frac{C_1 C_{eq1}}{C_1 + C_{eq1}} = \frac{12 \cdot 20}{12 + 20} = \frac{240}{32} = \frac{30}{4}$$

$$C_{eq2} = 7,5 \mu F$$

C_{eq2} و C_4 على التسلسل

$$C_{eq} = \frac{C_{eq2} \cdot C_4}{C_{eq2} + C_4} = \frac{7,5 \cdot 30}{30 + 7,5} = \frac{225}{37,5} = 6$$

$$C_{eq} = 6 \mu F$$

(2) - فرق الجهد V_{AB} , V_{BC} و V_{CD} وشحنة كل مكثفة:

$$Q_1 = C_{eq} \cdot V_{AD} = 6 \cdot 100 = 600 \mu C \Rightarrow Q_1 = 600 \mu C$$

$$V_{AB} = \frac{Q_1}{C_1} = \frac{600}{12} = 50 V \Rightarrow V_{AB} = 50 V$$

لدينا، $Q_4 = Q_1$ (الرابط على التسلسل).

$$Q_4 = 600 \mu C, V_{CD} = \frac{Q_4}{C_4} = \frac{600}{30} = 20 V$$

$$V_{CD} = 20 V$$

$$V_{BC} = V_{AD} - (V_{AB} + V_{CD}) = 100 - (50 + 20) = 30 V$$

(3)

$$V_{BC} = 30V$$

$$V_{BC} = V_2 = V_3 = 30V$$

(الربط على التفرع)

$$Q_2 = C_2 V_2 = 5 \cdot 30 = 150 \mu C$$

$$Q_2 = 150 \mu C$$

$$Q_3 = C_3 V_3 = 15 \cdot 30 = 450 \mu C \Rightarrow Q_3 = 450 \mu C$$

(3) - الطاقة المخزنة في الدارة

$$E_p = \frac{1}{2} C_{eq} V^2 = \frac{1}{2} \cdot 6 \times 10^{-6} \cdot (100)^2$$

$$E_p = 3 \times 10^{-4} J$$


- حل التقريبي (3):

1 - قانوني كيرسوف:

$$\Sigma I_n = 0 \quad \text{① - القانون الأول}$$

$$\Sigma E_n = 0 \quad \text{② - القانون الثاني}$$

2 - حساب التياران I_1 و I_2

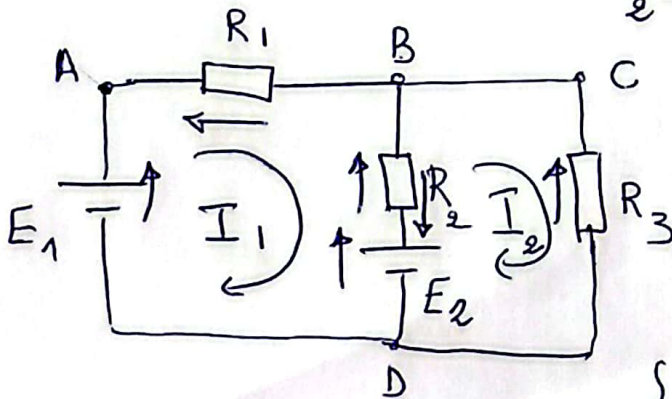

1 - نرسم الجهود على مستوى

كل عنصر

$$\Sigma V_n = 0 \quad \text{2 - نطبق}$$

$$\begin{cases} E_1 - R_1 I_1 - R_2 (I_1 - I_2) - E_2 = 0 \\ E_2 - R_2 (I_2 - I_1) - R_3 I_2 = 0 \end{cases}$$

(4)

$$\begin{cases} E_1 - E_2 - (R_1 + R_2)I_1 + R_2 I_2 = 0 \\ E_2 + R_2 I_1 - (R_2 + R_3)I_2 = 0 \end{cases}$$

$$\begin{cases} 4I_1 - 2I_2 = 4 \dots\dots (1) \\ -2I_1 + 3I_2 = 4 \dots\dots (2) \end{cases}$$

بضرب (2) × (2) نحصل على

$$4I_2 = 12 \Rightarrow \boxed{I_2 = 3A}$$

بالعوض في (1) نحصل على

$$4I_1 - 6 = 4 \Rightarrow I_1 = \frac{4+6}{4} = \frac{10}{4} = 2,5$$

$$\boxed{I_1 = 2,5A}$$


(3) - في الفرع AB : $I_1 = 2,5A$

الفرع CD : $I_2 = 3A$

الفرع BD : $I_3 = I_2 - I_1$

$$\boxed{I_3 = 0,5A}$$

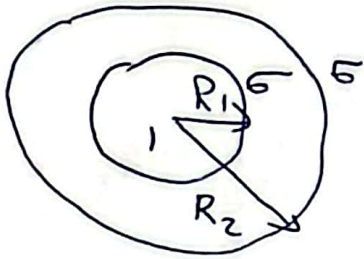(1) - باستخدام نظرية غاوس إيجاد الحقل الكهربائي



$$\oint \vec{E} \cdot d\vec{S} = \frac{\sum q}{\epsilon_0}$$

$$E \cdot S_g = \frac{q}{\epsilon_0}$$

$$E_1 \cdot S_g = 0 \Rightarrow E_1 = 0$$

$r < R_1 = R_2$ -

$$E_2 \cdot S_g = \frac{q}{\epsilon_0}$$

$R_1 < r < R_2 = R_2$ -

$$E_2 \cdot 4\pi r^2 = \frac{\sigma \cdot 4\pi R_1^2}{\epsilon_0} \Rightarrow$$

$$E_2 = \frac{\sigma R_1^2}{\epsilon_0 r^2}$$

$$E_3 \cdot S_g = \frac{\sum q_{int}}{\epsilon_0} = \frac{q_1 + q_2}{\epsilon_0}$$

$r > R_2 = R_2$ -

$$E_3 \cdot 4\pi r^2 = \frac{\sigma \cdot 4\pi R_1^2 + \sigma \cdot 4\pi R_2^2}{\epsilon_0}$$

$$E_3 = \frac{\sigma (R_1^2 + R_2^2)}{\epsilon_0 r^2}$$

(2) - عبارة الجهد الكهربائي

$$dV = - E \cdot dr$$

$$V = - \int E \cdot dr$$

$$V_3(r) = -\int E_3 \cdot dr = -\int \frac{\sigma(R_1^2 + R_2^2)}{\epsilon_0 r^2} dr \quad \text{for } r > R_2 \quad \text{---}$$

$$V_3(r) = \frac{\sigma(R_1^2 + R_2^2)}{\epsilon_0 r} + C_3.$$

$$\left. \begin{array}{l} V(\infty) = 0 \\ V_3(\infty) = C_3 \end{array} \right\} C_3 = 0 \quad \text{---}$$

$$\boxed{V_3(r) = \frac{\sigma(R_1^2 + R_2^2)}{\epsilon_0 r}}$$

$$V_2(r) = -\int E_2 dr = -\int \frac{\sigma R_1^2}{\epsilon_0 r^2} dr \quad \text{for } R_1 < r < R_2 \quad \text{---}$$

$$V_2(r) = \frac{\sigma R_1^2}{\epsilon_0 r} + C_2, \quad V_3(r=R_2) = V_2(r=R_2)$$

$$\frac{\sigma(R_1^2 + R_2^2)}{\epsilon_0 R_2} = \frac{\sigma R_1^2}{\epsilon_0 R_2} + C_2 \quad \text{---}$$

$$\frac{\cancel{\sigma R_1^2}}{\epsilon_0 R_2} + \frac{\sigma R_2^2}{\epsilon_0 R_2} - \frac{\cancel{\sigma R_1^2}}{\epsilon_0 R_2} = C_2 \Rightarrow \boxed{C_2 = \frac{\sigma R_2}{\epsilon_0}}$$

$$\boxed{V_2(r) = \frac{\sigma R_1^2}{\epsilon_0 r} + \frac{\sigma R_2}{\epsilon_0}}$$

$$V_1(r) = -\int E_1 \cdot dr = C_1 \quad \text{for } r < R_1 \quad \text{---}$$

$$V_1(r) = C_1, \quad V_1(r=R_1) = V_2(r=R_1)$$

$$C_1 = \frac{\sigma R_1^2}{\epsilon_0 R_1} + \frac{\sigma R_2}{\epsilon_0} = \frac{\sigma R_1}{\epsilon_0} + \frac{\sigma R_2}{\epsilon_0} = \frac{\sigma}{\epsilon_0} (R_1 + R_2)$$

$$\boxed{V_1(r) = \frac{\sigma}{\epsilon_0} (R_1 + R_2)}$$

(7)